

Please corr
table and t


x	00	01	11	10
0	0	0	0	0
1	0	1	0	1

$$F = xz + xy + yz$$


x	00	01	11	10
0	0	1	0	1
1	1	0	0	0

$$G = \overline{x}\overline{z} + \overline{x}\overline{y} + \overline{yz}$$

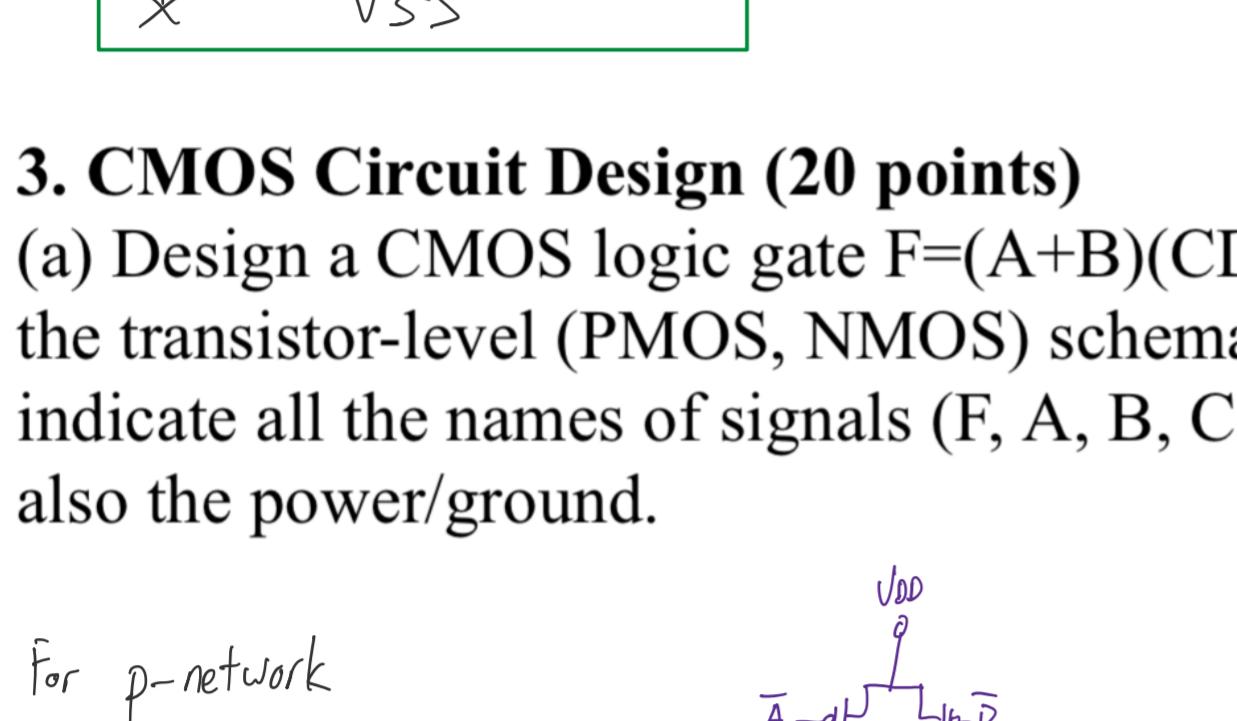2. Draw a layout for an ordering of input nets (15 points)
One slice shows a transistor design and a possible stick layout (please see a picture below)



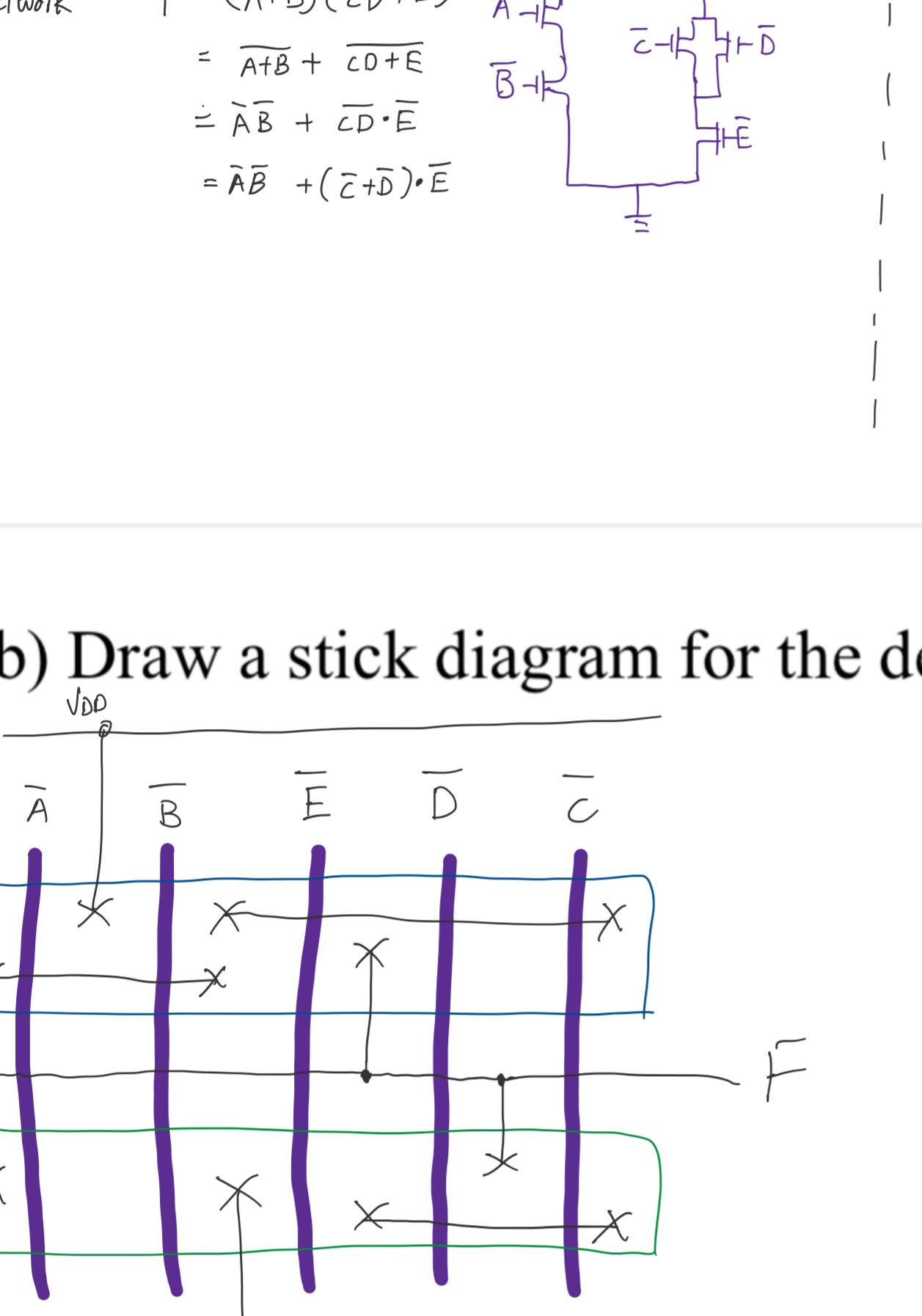Now if the input gate ordering is changed to a, b, c, d, e , please draw a new stick layout. Then, compare what you newly get with the above result and comment.




3. CMOS Circuit Design (20 points)

(a) Design a CMOS logic gate $F=(A+B)(CD+E)$. Draw the transistor-level (PMOS, NMOS) schematic. Please indicate all the names of signals (F, A, B, C, D, E) and also the power/ground.


For p-network

$$F = (A+B)(CD+E)$$


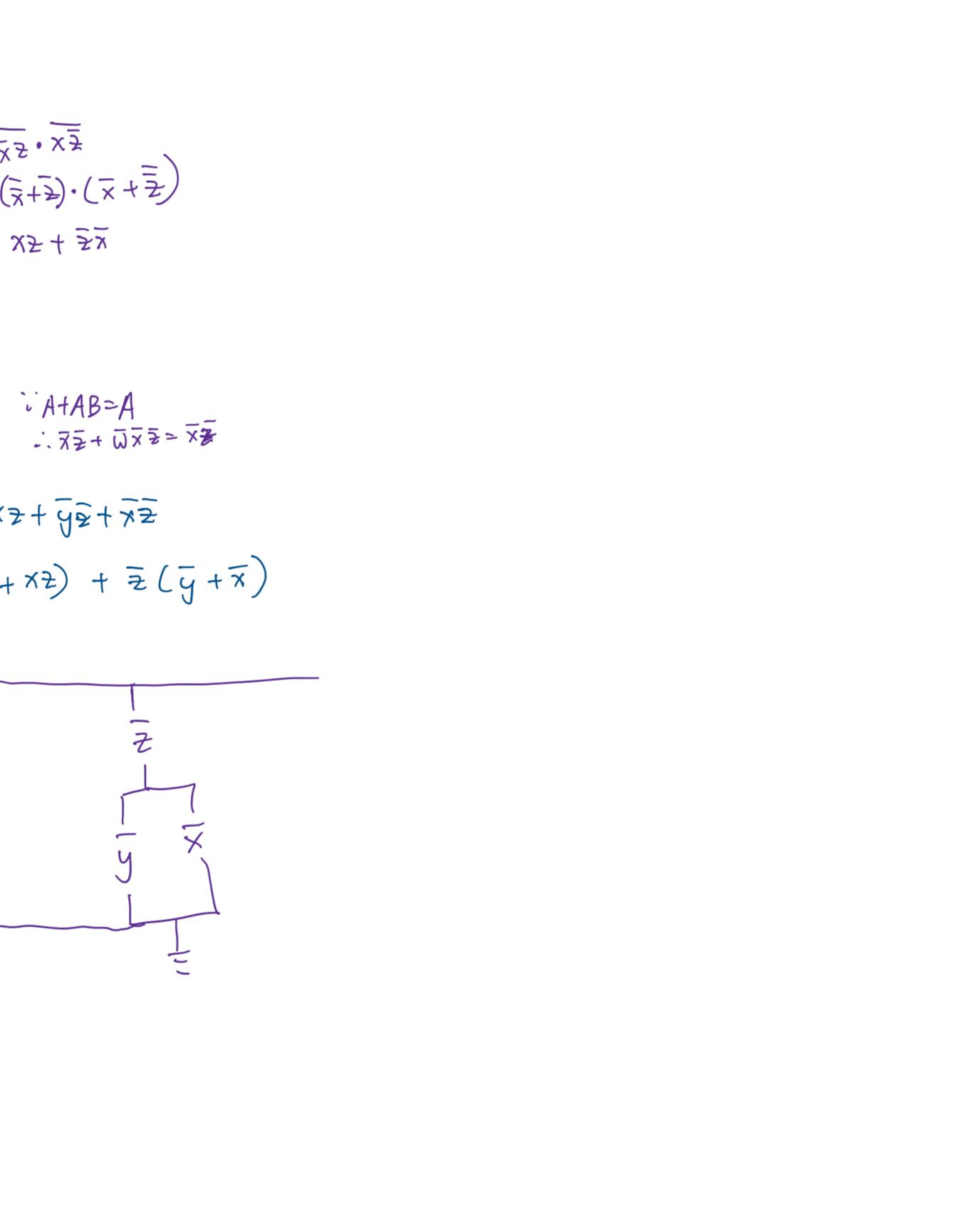
Inver each Input, $F = (\overline{A}+\overline{B})(\overline{C}\overline{D}+\overline{E})$



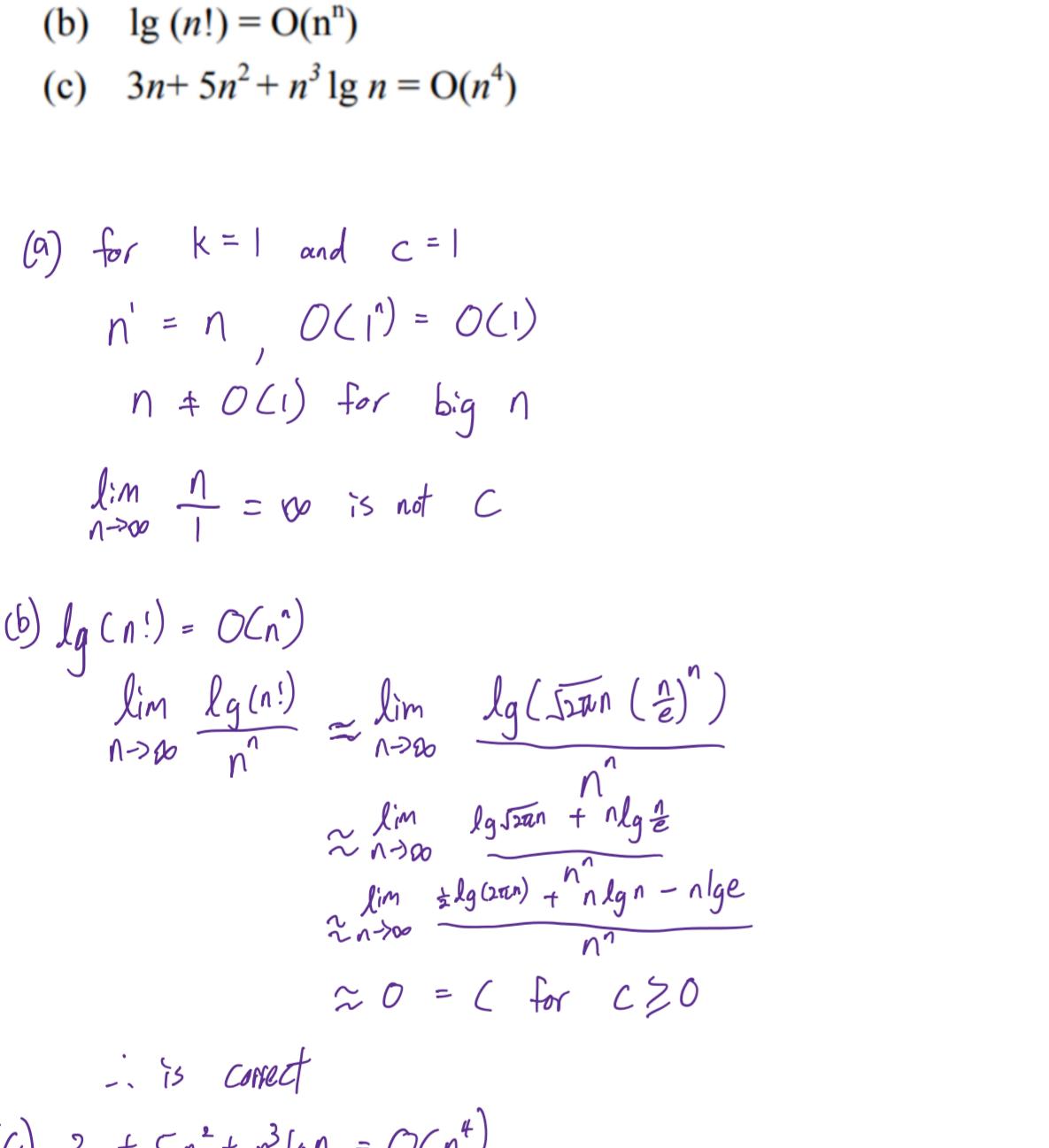(b) Draw a stick diagram for the design in (a).



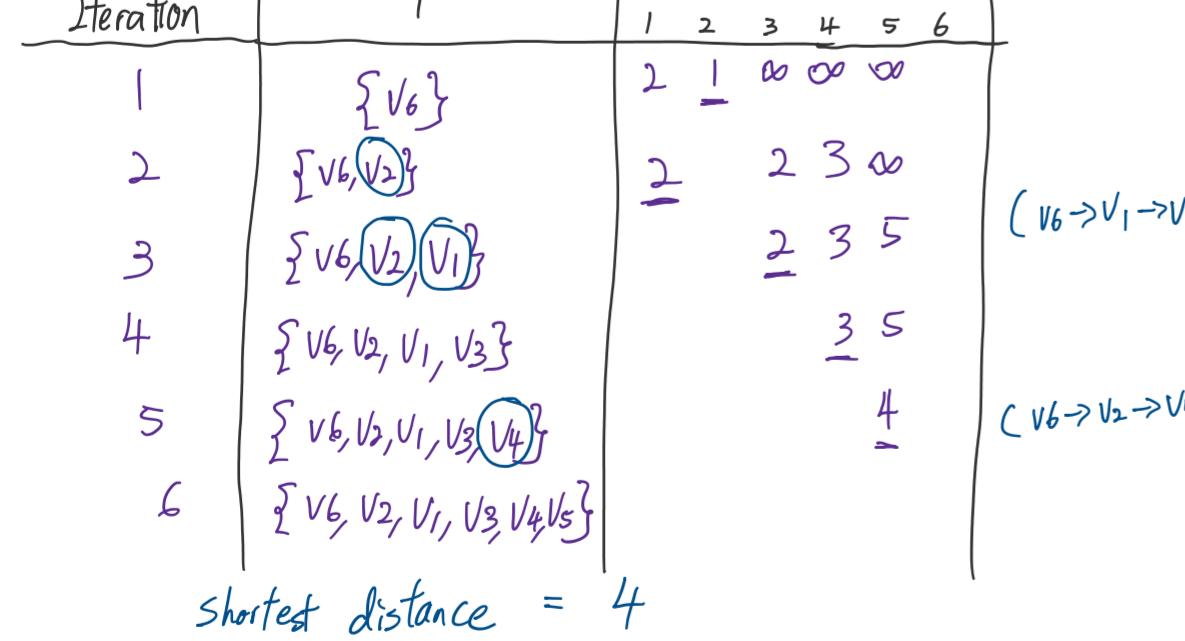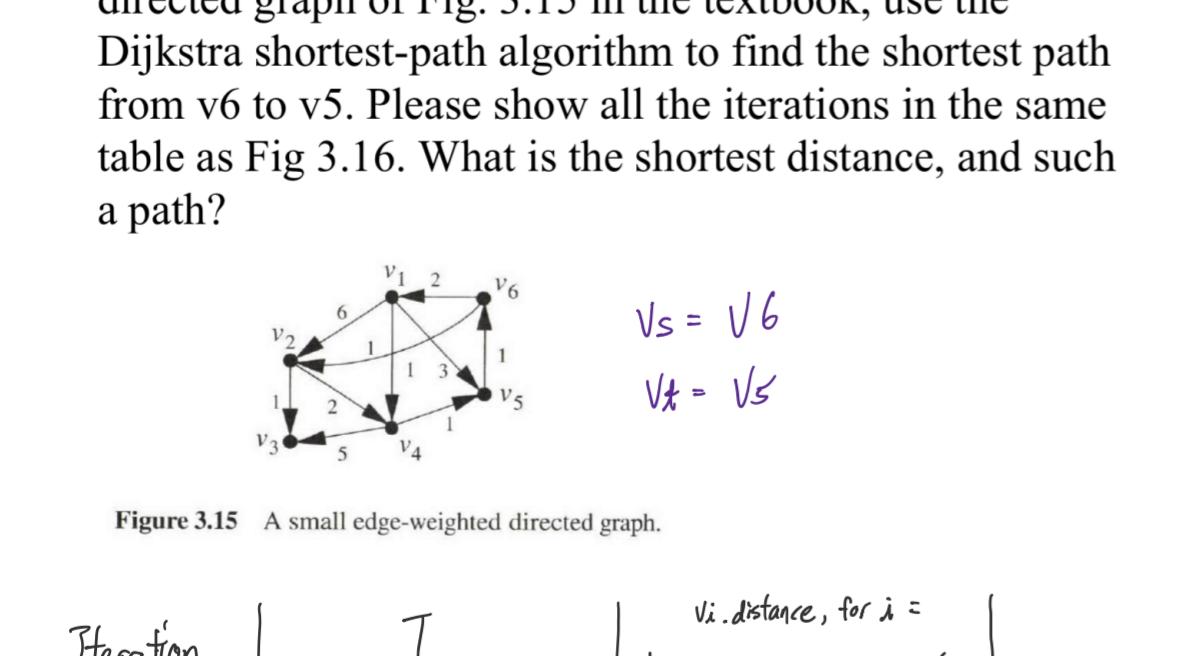(c) The following PMOS network was designed to implement the Boolean function $G(w,x,y,z)$. Please write the Boolean equation of G . Also complete the NMOS network.




4. Computation Complexity (5 points) Determine which of the following is correct.


$$(a) n^k = O(c^n), k \geq 1 \text{ and } c \geq 1.$$

$$(b) \lg(n!) = O(n^k)$$

$$(c) 3n + 5n^2 + n^3 \lg n = O(n^4)$$

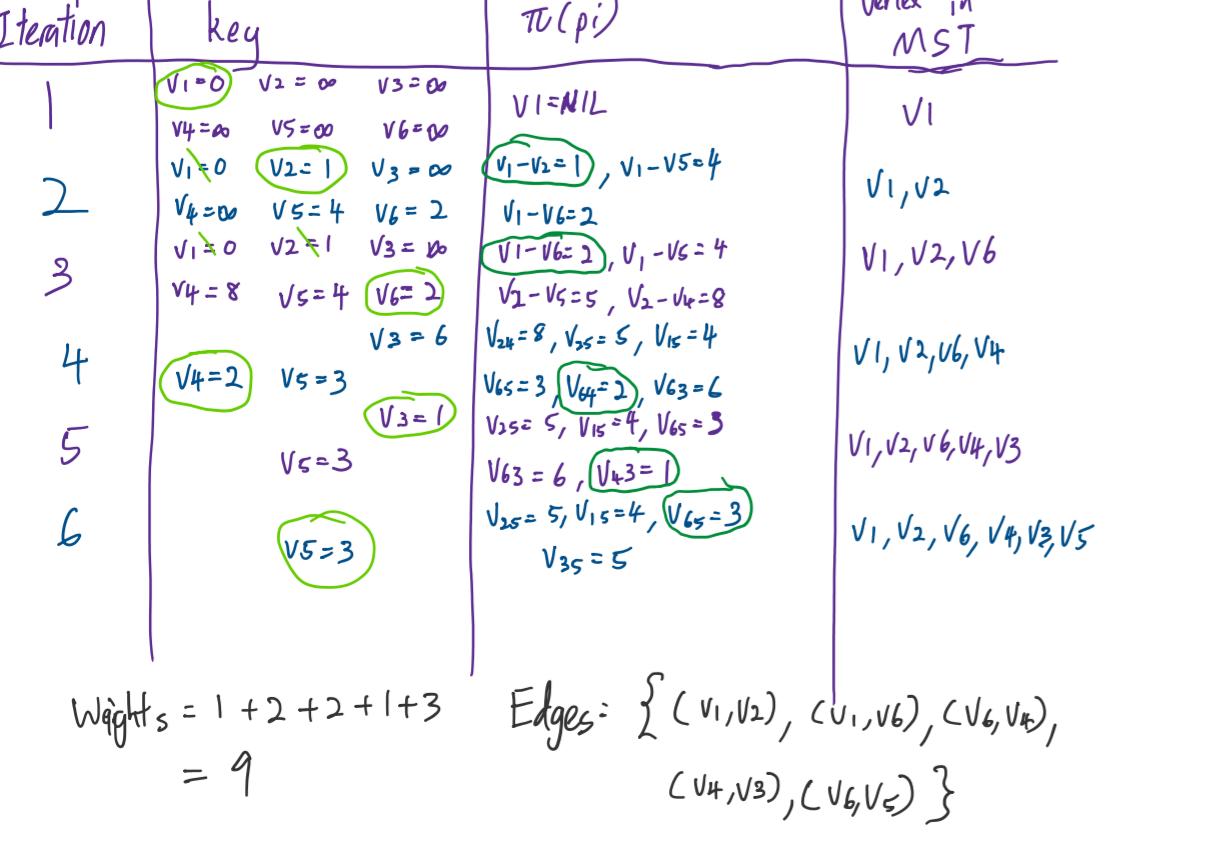

6. Prim's Algorithm for MST (15 points)

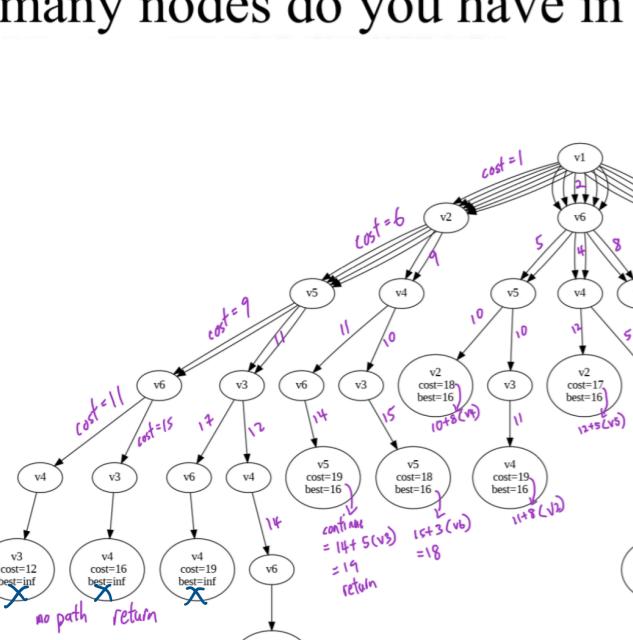

7. Branch and Bound (15 points)

Use the branch and bound algorithm to solve the TSP problem in above Figure HW-6. Start and end with $V1$. Show the search tree as Fig. 5.6 in the textbook. How many nodes do you have in your search tree?

